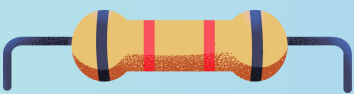


Audio Amplifier

AMPLIFIER

The amplifier circuit, which consists of a BJT that is **biased using a feedback resistor**, receives a low voltage input signal. This configuration yields a **gain of 57** for the stated input impedance in this stage.



BUFFER

In the CC Amplifier arrangement, an NPN transistor acts as the buffer. We have used a buffer at this stage of the circuit to **output the same voltage** and also for **impedance matching** that is fed into it from the potentiometer and the previous stage.


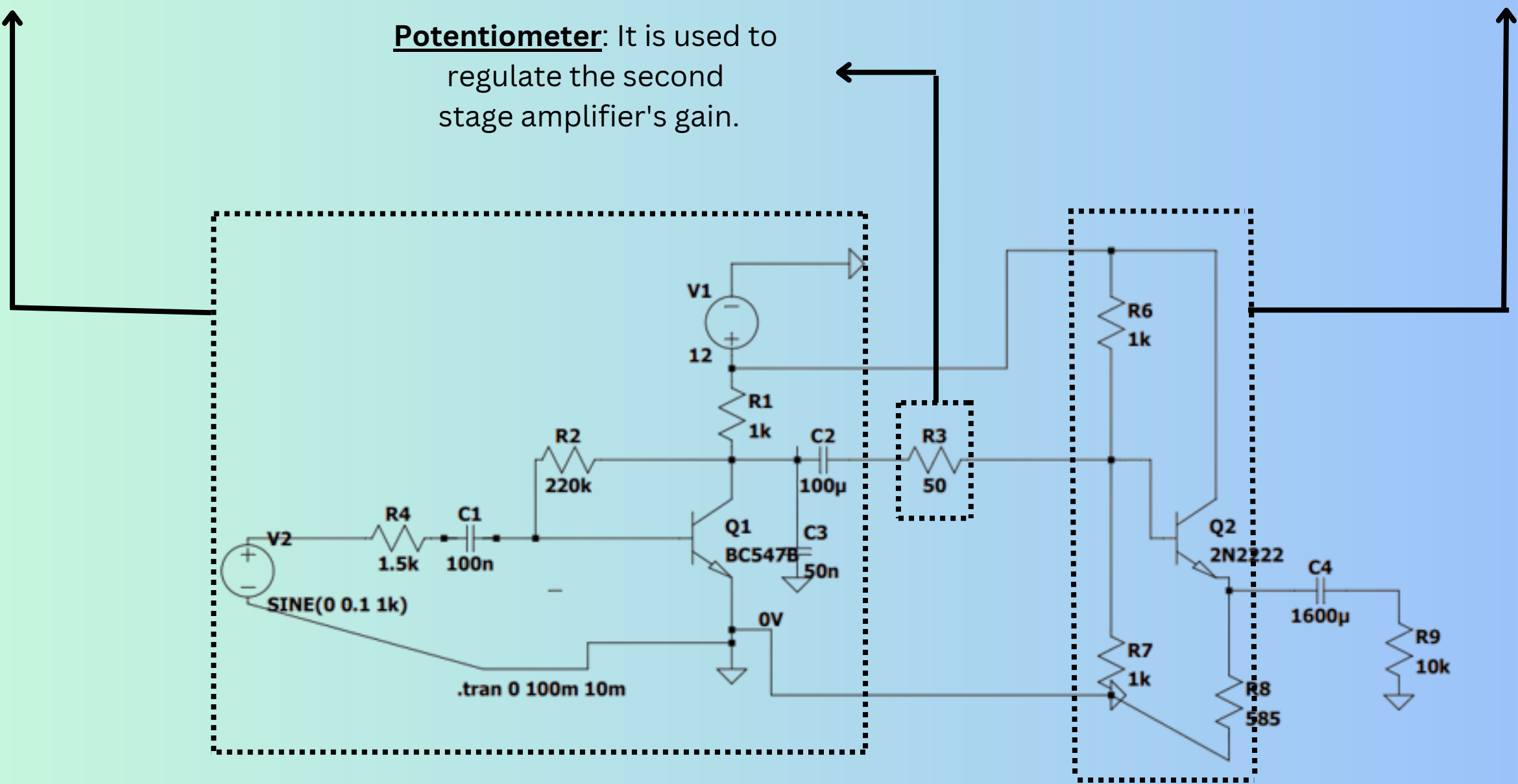


fig.Main circuit

Circuit Analysis

DC ANALYSIS

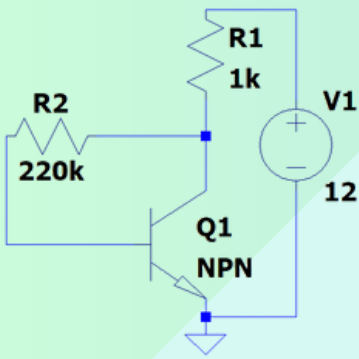

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_C}$$
$$\Rightarrow I_B = 23.9 \mu A$$
$$\text{And, } I_C = \beta \cdot I_B$$
$$\Rightarrow I_C = 5.9 \text{ mA}$$
$$g_m = \frac{I_C}{V_T} = 0.2285$$

$$A_{V_{be}} = \frac{V_o}{V_{be}}$$
$$\left\{ \frac{V_o}{V_{in}} = \frac{V_o}{V_{be}} \times \frac{V_{be}}{V_{in}} \right\}$$
$$\Rightarrow A_{V_{be}} = \frac{V_o}{V_{be}} = -g_m(R_C \parallel R_L)$$
$$\Rightarrow A_{V_{be}} = -226.9$$


Now, by Miller's Theorem:

$$R_1 = \frac{R_B}{1 - A_V}$$

$$\Rightarrow R_1 = 965 \Omega$$
$$\text{and, } r_{\pi} = \frac{\beta}{g_m}$$
$$\Rightarrow r_{\pi} = 1096.5 \Omega$$

Small Signal Model
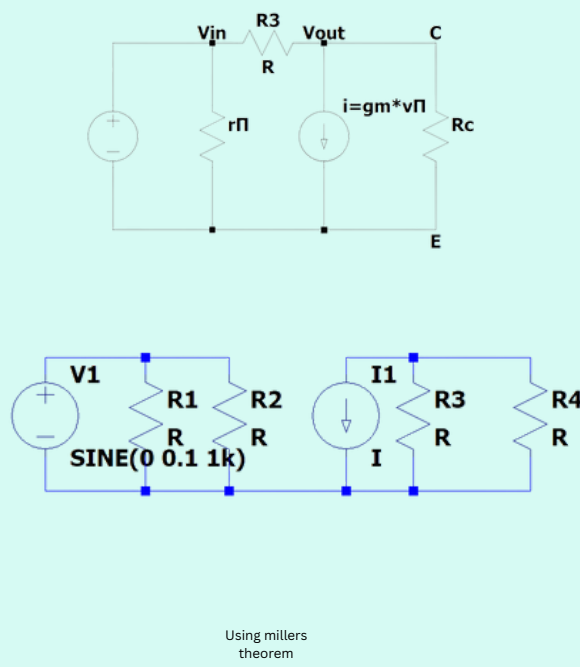
$$Z_{in} = 513.36 \Omega$$
$$\frac{V_{be}}{V_{in}} = \frac{Z_{in}}{Z_{in} + R_S}$$
$$= 0.254$$
$$\text{So, Gain} = 226.9 \times 0.254 = 57.63$$



Using millers theorem

OBSERVATION:

The Circuit is Successfully tested and verified on both Ltspice and oscilloscope.

APPLICATIONS:

- In various instruments that relate to music, these amplifiers are installed.
- For the wireless transmission of the signals, audio amplification is required.